

EE 310 - LAB 3

State Variables

Step1:

Consider the circuit in Figure 1, Determine the state-Space representation of the circuit.

Where v_s is the input and i_x is the output. Take $R = 1\Omega$, $C = 0.25 F$, and $L = 0.5 H$.

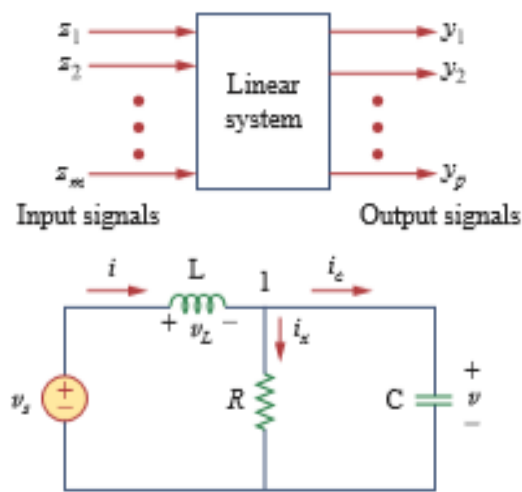


Figure 1

Step2:

We want to use Simulink for simulating the state space model found in step1.

- Use **step input signal** and find simulation results
- Use **ramp input signals** and find simulation results
- Use **sinusoidal input signal** and find simulation results.

HINT: Use the following blocks in the Simulink Library Browser




Step



Ramp



Sine Wave

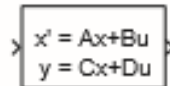

State-Space



Scope

$$\dot{x} = Ax + Bz$$

$$y = Cx + Dz$$

Solution of first model:

Solution:

We select the inductor current i and capacitor voltage v as the state variables.

$$v_L = L \frac{di}{dt} \quad (16.10.1)$$

$$i_C = C \frac{dv}{dt} \quad (16.10.2)$$

Applying KCL at node 1 gives

$$i = i_x + i_C \rightarrow C \frac{dv}{dt} = i - \frac{v}{R}$$

or

$$\dot{v} = -\frac{v}{RC} + \frac{i}{C} \quad (16.10.3)$$

since the same voltage v is across both R and C . Applying KVL around the outer loop yields

$$v_s = v_L + v \rightarrow L \frac{di}{dt} = -v + v_s$$
$$i = -\frac{v}{L} + \frac{v_s}{L} \quad (16.10.4)$$

Equations (16.10.3) and (16.10.4) constitute the state equations. If we regard i_x as the output,

$$i_x = \frac{v}{R} \quad (16.10.5)$$

Putting Eqs. (16.10.3), (16.10.4), and (16.10.5) in the standard form leads to

$$\begin{bmatrix} \dot{v} \\ \dot{i} \end{bmatrix} = \begin{bmatrix} -\frac{1}{RC} & \frac{1}{C} \\ -\frac{1}{L} & 0 \end{bmatrix} \begin{bmatrix} v \\ i \end{bmatrix} + \begin{bmatrix} 0 \\ \frac{1}{L} \end{bmatrix} v_s \quad (16.10.6a)$$

$$i_x = \begin{bmatrix} \frac{1}{R} & 0 \end{bmatrix} \begin{bmatrix} v \\ i \end{bmatrix} \quad (16.10.6b)$$